

10/10/19

# Digital Electronics




## Sequential Circuits

→ to hold a value 0/1


★ SR Latch → NAND  
NOR

clk = clock  
(digital signal)

★ SR Flip Flop

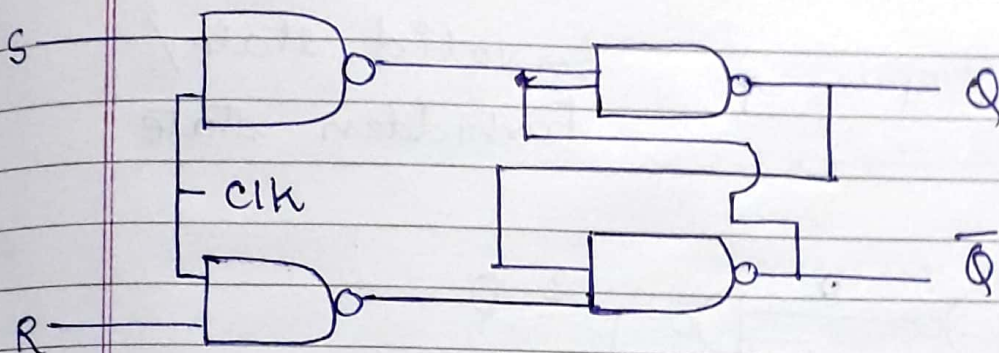


S	R	clk	Q   $\bar{Q}$
x	x	0	No change in o/p Previous state

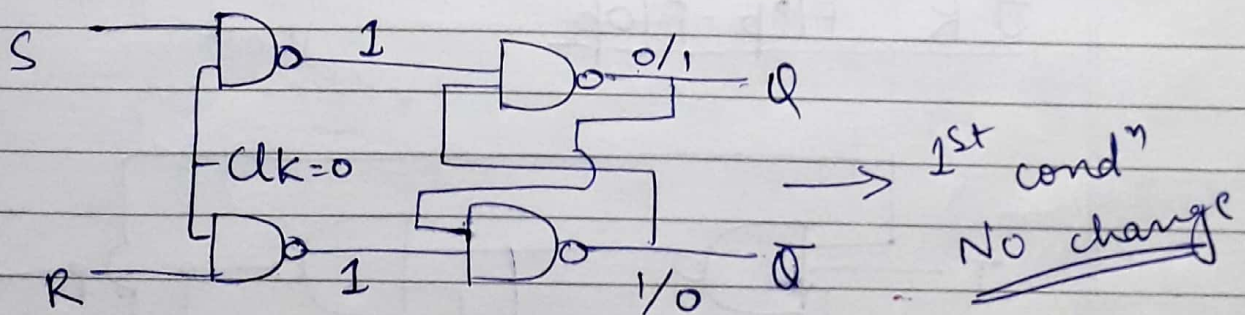


# Flip-Flop $\rightarrow$ storage dets

S	R	clk	Q	$\bar{Q}$
x	x	0	No change in o/p	
0	0	1	No change in o/p	
0	1	1	0	1
1	0	1	1	0
1	1	1	Invalid state/ Forbidden state	

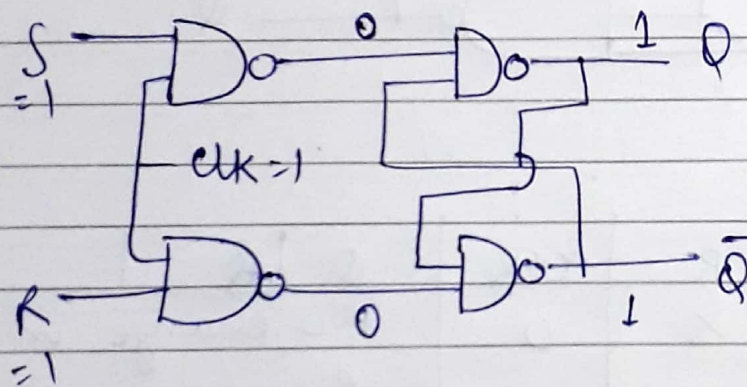

last  
Case

## J K Flip-Flop

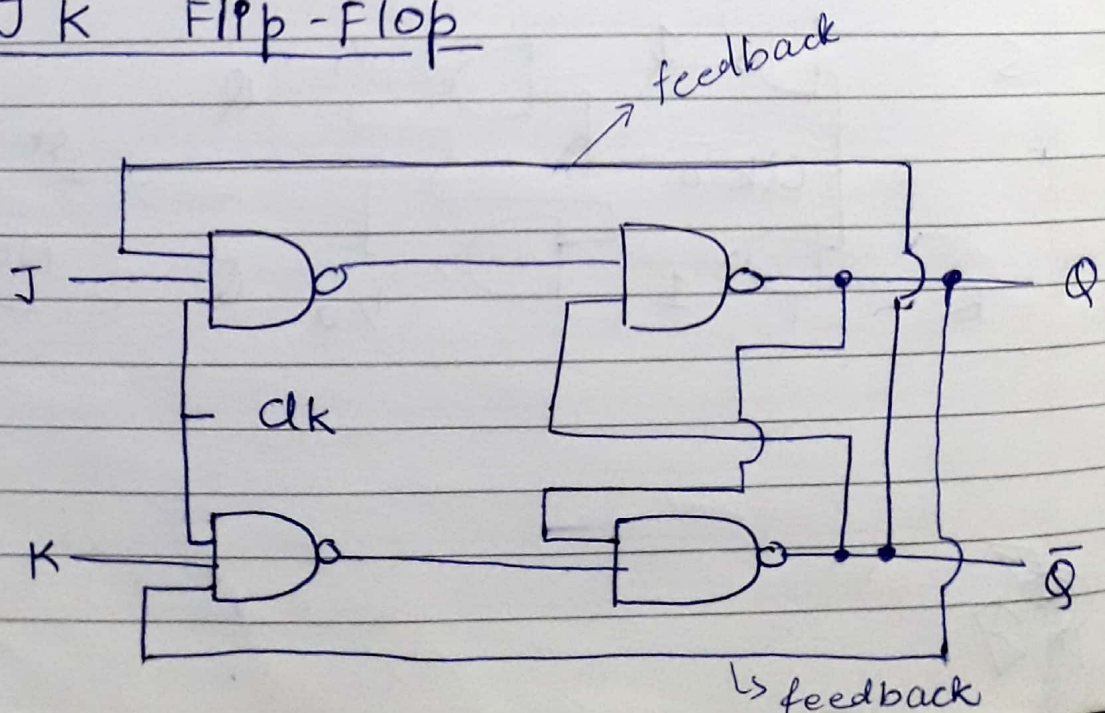





J	K	clk	Q	$\bar{Q}$
X	X	0	Previous state	
0	0	1	Previous state	
0	1	1	0	1
1	0	1	1	0
1	1	1	Toggle o/p (Race around)	

in these  
 cycles will  
 move till  
 the final  
 o/p

assume  
 $Q = 0$  &  
 $\bar{Q} = 1$  at  
 first.

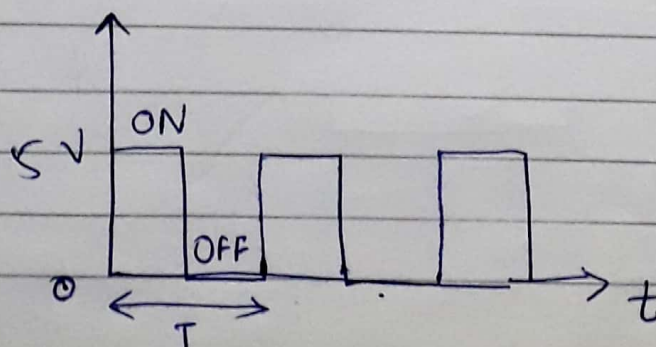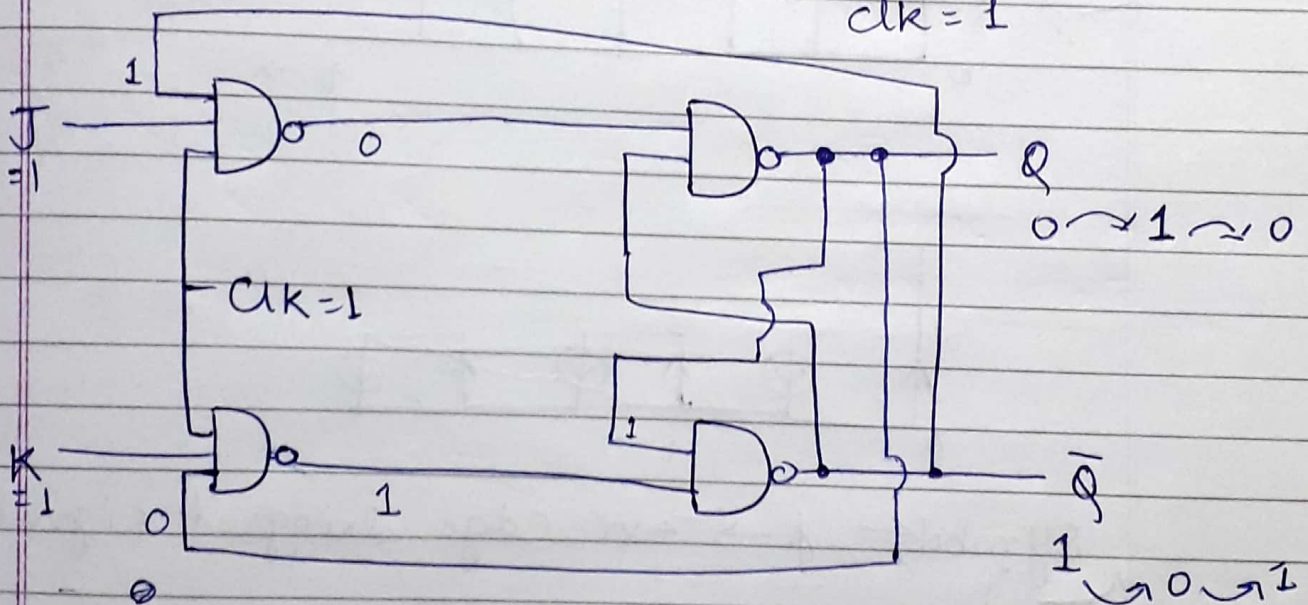"uncertain cond"  
 this will happen till  
 $clk = 1$



## Propagation time

clock

giving I/P



level triggering

edge triggering

{ ——— clk Positive level triggered signal  
 ○ ——— clk negative level triggered signal

> ——— clk → edge triggered signal (+ve)

○ ——— clk edge triggered (-ve)

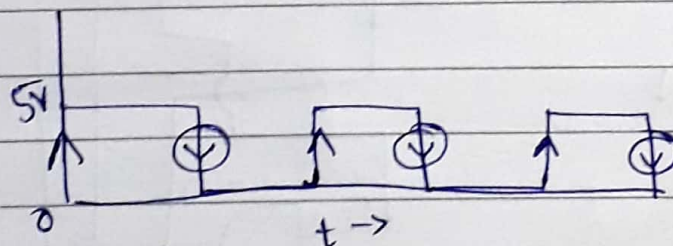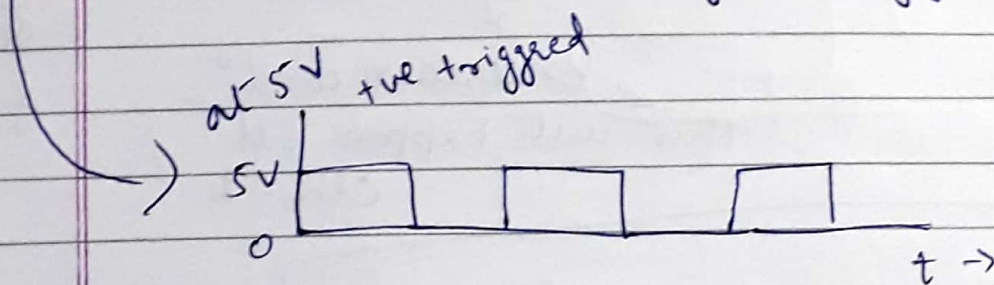


Symbol ← ↑ → +ve edge triggered signal  
(>)

⊕ → -ve edge triggered signal  
(⊕)



# ★ Masters Slave JK flip flop

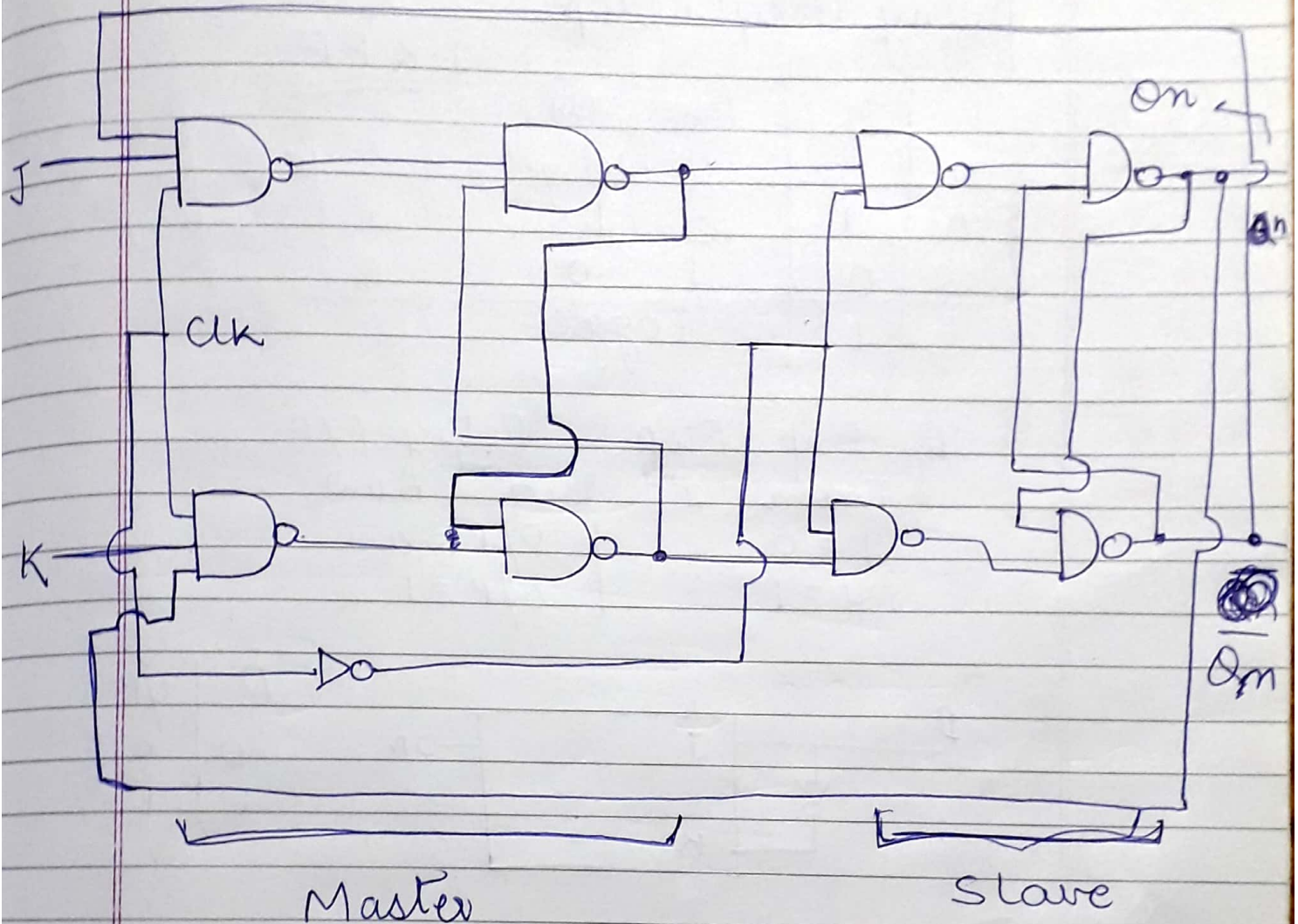


J	K	Qn
0	0	No change
0	1	0
1	0	1
1	1	$\overline{Qn}$

# Flip-Flop Conversions


## Delay Flip-Flop

J	K	On	On	<u>J-K FF</u>
0	0	No change		
0	1	0	1	
1	0	1	0	
1	1	Toggle		

D Flip Flop      Delay F/F  
 From 2<sup>nd</sup> & 3<sup>rd</sup> Row  
 J = 0      |      O/P = 0  
 J = 1      |      O/P = 1

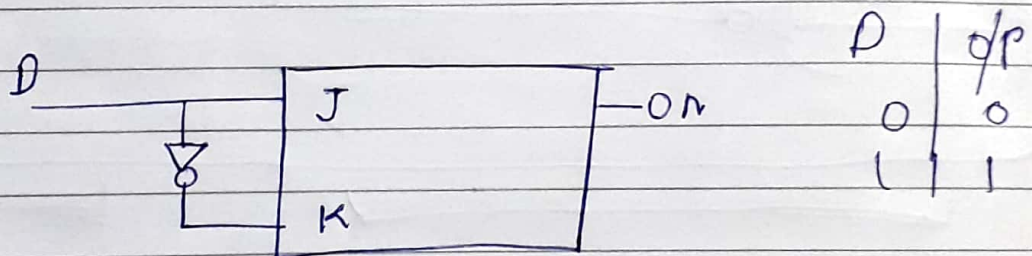


## Toggle T-Flip Flop

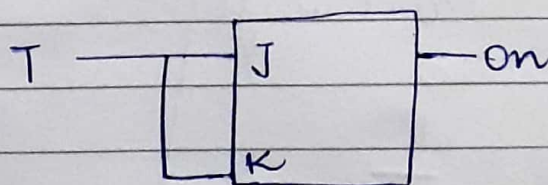

T	On
0	Previous
1	Toggle



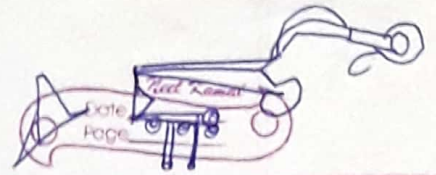

## Flip-Flop conversions

SR Flip-Flop to T flip flop

Truth table / Excitation table for Modified T-flip-flop

T	Present state $Q_n$	next state $Q_{n+1}$	S	R	$S_{m}$	$R_{m}$
0	0	0	0	1	0	x
0	1	1	0	0	x	0
1	0	1	1	0	1	0
1	1	0	0	1	0	1

always see the next state o/p

K-map for S


on \ T	0	1
0	0	1 <sub>2</sub>
1	x <sub>1</sub>	0 <sub>3</sub>

K-map for R

on \ T	0	1
0	x <sub>1</sub>	0 <sub>2</sub>
1	0 <sub>1</sub>	1 <sub>3</sub>

$$S = T \bar{Q}_n$$

$$R = T Q_n$$

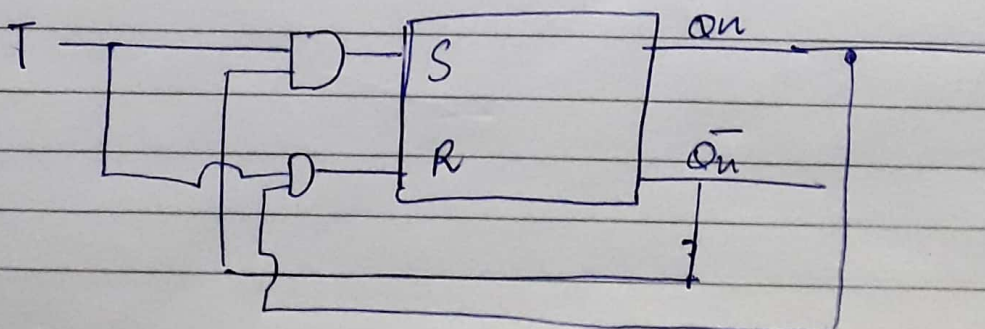

SR flip-flop to D-flip-flop

D	$Q_n$	$\bar{Q}_n$	S	R	Modified	
					S	R
0	0	0	0	1	0	x
<del>0</del>			0	0		
1	1	1	1	0	x	0
<del>1</del>			0	0		